

PODATKI ZA VAJO 1, NALOGA 2

NALOGA 2.1

$$\begin{aligned} U &= \frac{19}{1} \text{ V} \\ U_1 &= \frac{8,67}{1} \text{ V} \\ R_1 &= \frac{47}{1} \text{ k}\Omega \end{aligned}$$

NALOGA 2.2

$$\begin{aligned} U &= \frac{11}{1} \text{ V} \\ I &= \frac{207,5}{1} \mu\text{A} \\ I_1 &= \frac{73,33}{1} \mu\text{A} \\ R_1 &= \frac{150}{1} \text{ k}\Omega \end{aligned}$$