

# Mechatronic Actuators

## Lecture 5a

# Asynchronous motors

# Pointers

- Basics

$$A \cos(\omega t + \varphi) = \operatorname{Re} \left[ A e^{j(\omega t + \varphi)} \right] = \operatorname{Re} \left[ A e^{j\varphi} A e^{j(\omega t)} \right]$$

- Transformation

$$x(t) = A \cos(\omega t + \varphi) \rightarrow \mathbf{X}(j\omega) = A e^{j\varphi}$$

# Impedance

- Definition

$$Z = \frac{\mathbf{U}(j\omega)}{\mathbf{I}(j\omega)}$$

- Resistor impedance

$$i(t) = \frac{U(t)}{R} = \frac{A}{R} \cos(\omega t)$$

$$Z_R = \frac{\mathbf{U}(j\omega)}{\mathbf{I}(j\omega)} = \frac{Ae^{j0}}{\frac{A}{R}e^{j0}} = R$$

# Coil impedance

- Current across the coil

$$i(t) = \frac{1}{L} \int U dt = \frac{A}{L\omega} \sin(\omega t) = \frac{A}{L\omega} \cos\left(\omega t - \frac{\pi}{2}\right)$$

- Pointer

$$\frac{A}{L\omega} e^{-j\frac{\pi}{2}}$$

- Coil impedance

$$Z_L = \frac{\mathbf{U}(j\omega)}{\mathbf{I}(j\omega)} = \frac{Ae^{j0}}{\frac{A}{L\omega} e^{-j\frac{\pi}{2}}} = \frac{A}{-j\frac{A}{L\omega}} = j\omega L$$

# Capacitor impedance

- Current across the capacitor

$$i(t) = C \frac{dU}{dt} = -CA\omega \sin(\omega t) = -CA\omega \cos\left(\omega t - \frac{\pi}{2}\right)$$


- Pointer

$$-CA\omega e^{j\frac{\pi}{2}}$$

- Capacitor impedance

$$Z_C = \frac{U(j\omega)}{I(j\omega)} = \frac{Ae^{j0}}{-CA\omega e^{-j\frac{\pi}{2}}} = \frac{1}{j\omega C}$$

# 3-phase voltage

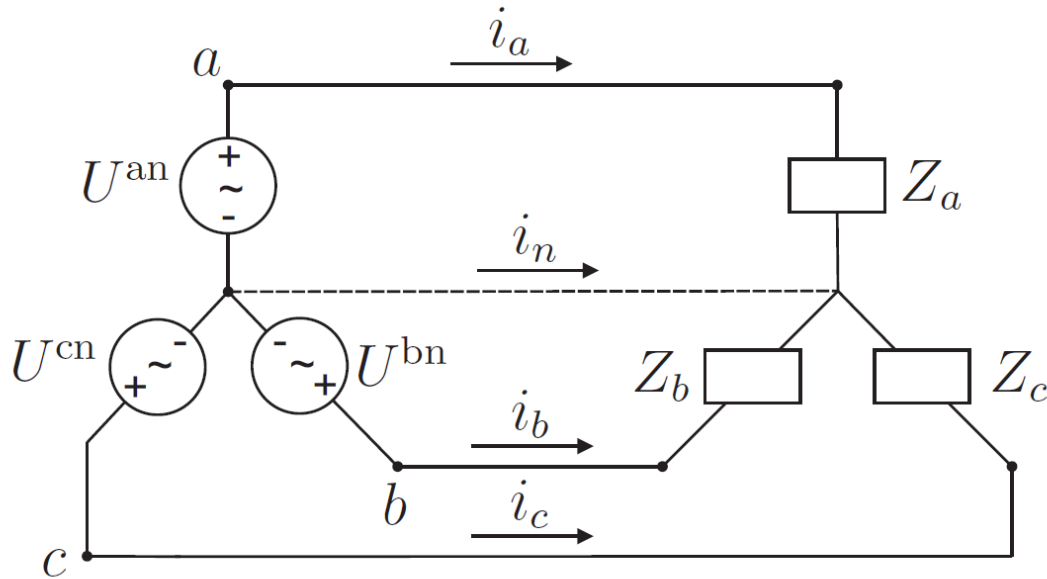

$$U_{ef}^{an}(j\omega) = U_{ef}^{an} \angle 0^\circ$$

$$U_{ef}^{bn}(j\omega) = U_{ef}^{bn} \angle -120^\circ$$

$$U_{ef}^{cn}(j\omega) = U_{ef}^{cn} \angle -240^\circ = U_{ef}^{cn} \angle 120^\circ$$

# Characteristics of 3-phase voltage

- Power on load that is not just pure resistance

$$P(t) = U(t)i(t) = U_0 \cos(\omega t) i_0 \cos(\omega t - \varphi) = U_0 i_0 \frac{1}{2} [\cos \varphi + \cos(2\omega t - \varphi)]$$

- Average power

$$\bar{P} = \frac{U_0 i_0}{2} \cos \varphi = U_{\text{ef}} i_{\text{ef}} \cos \varphi = \frac{U_{\text{ef}}^2}{|Z|} \cos \varphi = i_{\text{ef}}^2 |Z| \cos \varphi$$

- Current power on three phases (resistors only)

$$P(t) = P_a(t) + P_b(t) + P_c(t) = \frac{U_{\text{ef}}^2}{R} [1 + \cos(2\omega t)] + \frac{U_{\text{ef}}^2}{R} [1 + \cos(2\omega t - 120^\circ)] + \frac{U_{\text{ef}}^2}{R} [1 + \cos(2\omega t + 120^\circ)] = \frac{3U_{\text{ef}}^2}{R}$$